

**Birla Institute of Technology and Science Pilani**  
**CS F342 Computer Architecture**  
**Second Semester 2017-18**  
**Homework Exercise – 2 (23<sup>rd</sup> January 2018)**

---

**Behavioral Modeling Style**

**HWP02:** Implement a **8-bit unsigned multiplier** using the shift-add algorithm. The module has two 8-bit unsigned inputs **a,b** a **clock** signal (negative edge), **reset** (active high, asynchronous) and a 16-bit output **prod** also there is a single bit output **eop** (end of operation) which goes high for one clock cycle when the multiplication operation is completed.

**HWP03:** Implement a **BCD up/down counter**. The counter has a two-digit output (remember each BCD digit is 4-bit wide and valid BCD digits are from 0 to 9 only). The counter counts from “00” to “59” if it is counting in **up** mode. It will count from “59” to “00” when it is in **down** mode. Choose a negative edge clock and asynchronous active low reset for the module. There is a control signal **up/down** which determines the mode of operation of the counter. **Up** when **high** and **down** when **low**.

Example output: count in up mode

00, 01, 02, 03, 04, 05, 06, 07, 08, 09, 10, 11, 12, 13 ..... 59, 00,01 ...

**HWP04:** Implement a **8-bit signed divider** using **repetitive subtraction**. The module has two 8-bit signed inputs **divisor, dividend** a **clock** signal (negative edge), **reset** (active high, asynchronous) and two 8-bit outputs **remainder and quotient** also there is a single bit output **eop** (end of operation) which goes high for one clock cycle when the division operation is completed.

\*\*\*\*\*